

$C_{GD}, C_{DB}, C_{GS}, C_{SB}, C_{GB}$


$M_1: C_{GD}, C_{SB}=0, C_{GS}$  与  $C_{GB}$  一致,  $C_{DB}$ .

$M_2: C_{GD}, C_{SB}=0, C_{GS}$  与  $C_{GB}$  一致,  $C_{DB}$

$M_3: C_{GD}=0, C_{SB}=0, C_{DB}$  与  $C_{GB}$  与  $C_{GS}$  一致 从 G/B 到 S/B.

$M_4: C_{GD}=0, C_{SB}=0, C_{DB}$  与  $C_{GB}$  与  $C_{GS}$  一致.

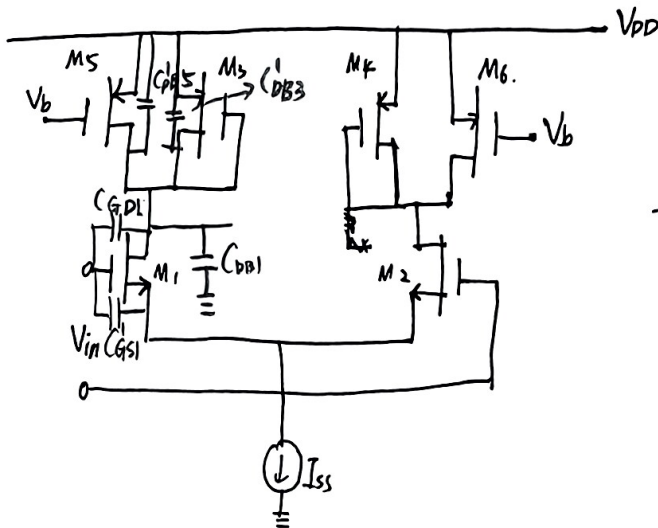$M_5: C_{SB}=0, C_{GS}=0, C_{GB}=0, C_{DB}$  与  $C_{GD}$  一致  
故补充电容后电路如下图所示:



其中  $C'_{DB5} = C_{DB5} + C_{GD5}$


$C'_{DB3} = C_{DB3} + C_{GB3} + C_{GS3}$

$C'_{GS1} = C_{GS1} + C_{GB1}$

故  $C'_{DB5}$  与  $C'_{DB3}$  可合并为  $C'_{DB}$   
与  $C_{DB1}$

进而利用半边电路法有:




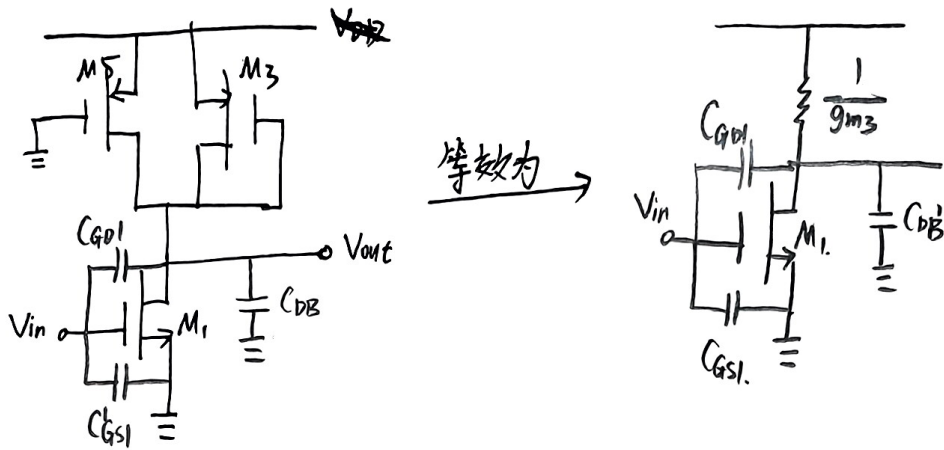

考虑  $R_s$  和  $C_L$  得:

其中  $C'_L = C_L + C'_{DB}$

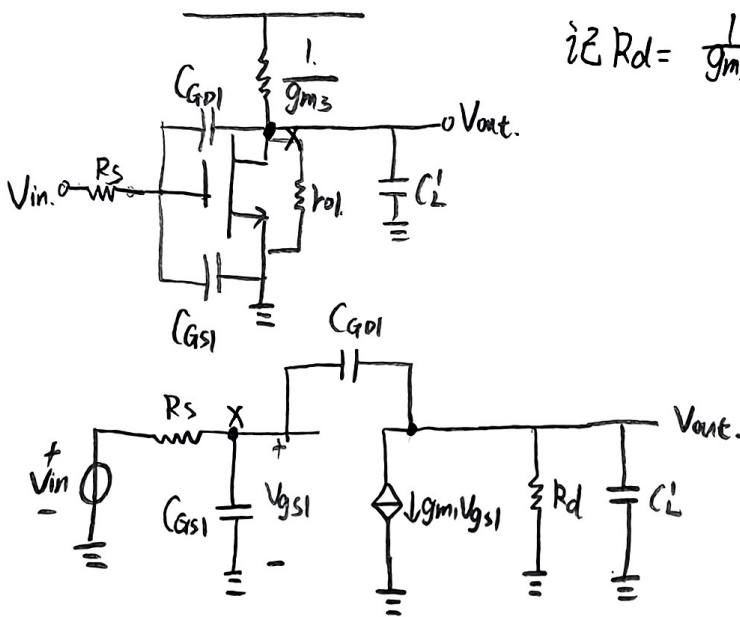记  $R_d = \frac{1}{g_{m3}} \parallel r_{o1}$



$$\text{KCL: } \textcircled{1} \frac{V_{in} - V_x}{R_s} = \frac{V_x - V_{out}}{\frac{1}{C_{gd1}s}} + \frac{V_x - 0}{\frac{1}{C_{gs1}s}}$$

$$\textcircled{2} \frac{V_x - V_{out}}{\frac{1}{C_{db1}s}} = g_{m1} V_x + \frac{V_{out}}{R_d} + \frac{V_{out}}{\frac{1}{C'_L s}}$$

联立得:

$$\frac{V_{out}}{V_{in}} = \frac{(C_{gd1}s - g_{m1})R_d}{A s^2 + B s + C}$$

$$\begin{cases} A = R_s R_d [C_{gd1} \cdot C_{gs1} + C_{gd1} \cdot C'_L + (C_{gs1} \cdot C'_L)] \\ B = (C_{gd1} + C_{gs1}) R_s + (C_{gd1} + C'_L) R_d + g_{m1} R_s R_d C_{gd1} \\ C = 1 \end{cases}$$

